

Laboratory Exercise 10

An Enhanced Processor

In Laboratory Exercise 9 we described a simple processor. In Part I of that exercise the processor itself was designed, and in Part II the processor was connected to an external counter and a memory unit. This exercise describes subsequent parts of the processor design. Note that the numbering of figures and tables in this exercise are continued from those in Parts I and II of the preceding lab exercise.

Part III

In this part you will extend the capability of the processor so that the external counter is no longer needed, and so that the processor has the ability to perform read and write operations using memory or other devices. You will add three new types of instructions to the processor, as displayed in Table 3. The **ld** (load) instruction loads data into register R_X from the external memory address specified in register R_Y . The **st** (store) instruction stores the data contained in register R_X into the memory address found in R_Y . Finally, the instruction **mvnz** (move if not zero) allows a **mv** operation to be executed only under the condition that the current contents of register G are not equal to 0.

Operation	Function performed
ld $R_X, [R_Y]$	$R_X \leftarrow [[R_Y]]$
st $R_X, [R_Y]$	$[R_Y] \leftarrow [R_X]$
mvnz R_X, R_Y	if $G \neq 0$, $R_X \leftarrow [R_Y]$

Table 3: New instructions performed in the processor.

A schematic of the enhanced processor is given in Figure 11. In this figure, registers R_0 to R_6 are the same as in Figure 1 of Laboratory Exercise 9, but register R_7 has been changed to a counter. This counter is used to provide the addresses in the memory from which the processor's instructions are read; in the preceding lab exercise, a counter external to the processor was used for this purpose. We will refer to R_7 as the processor's *program counter* (PC), because this terminology is common for real processors available in the industry. When the processor is reset, PC is set to address 0. At the start of each instruction (in time step 0) the contents of PC are used as an address to read an instruction from the memory. The instruction is stored in IR and the PC is automatically incremented to point to the next instruction (in the case of **mvi** the PC provides the address of the immediate data and is then incremented again).

The processor's control unit increments PC by using the *incr_PC* signal, which is just an enable on this counter. It is also possible to directly load an address into PC (R_7) by having the processor execute a **mv** or **mvi** instruction in which the destination register is specified as R_7 . In this case the control unit uses the signal R_{7in} to perform a parallel load of the counter. In this way, the processor can execute instructions at any address in memory, as opposed to only being able to execute instructions that are stored in successive addresses. Similarly, the current contents of PC can be copied into another register by using a **mv** instruction. An example of code that uses the PC register to implement a loop is shown below, where the text after the % on each line is just a comment. The instruction **mv** R_5, R_7 places into R_5 the address in memory of the instruction **sub** R_4, R_2 . Then, the instruction **mvnz** R_7, R_5 causes the **sub** instruction to be executed repeatedly until R_4 becomes 0. This type of loop could be used in a larger program as a way of creating a delay.

```

mvi  R2,#1
mvi  R4,#10000000 % binary delay value
mv   R5,R7        % save address of next instruction
sub  R4,R2         % decrement delay count
mvnz R7,R5         % continue subtracting until delay count gets to 0

```

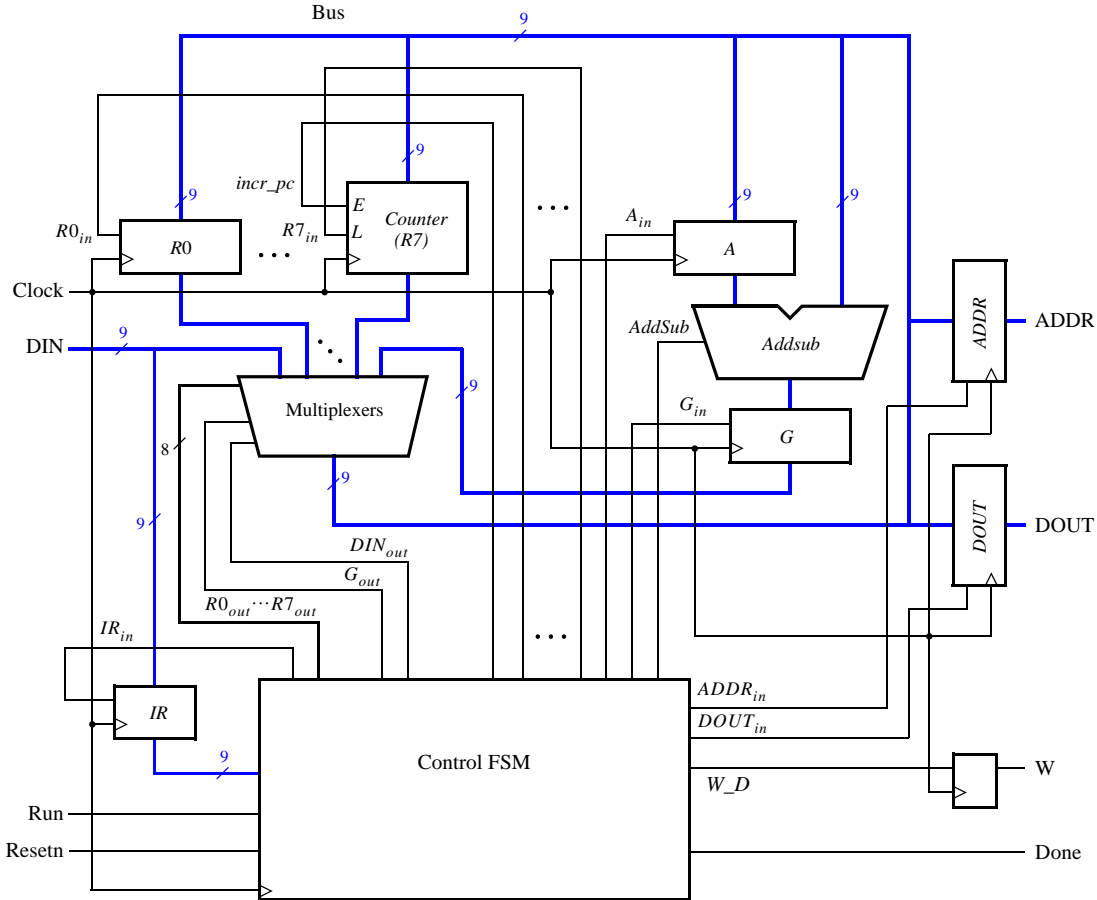


Figure 11: An enhanced version of the processor.

Figure 11 shows two registers in the processor that are used for data transfers. The *ADDR* register is used to send addresses to an external device, such as a memory module, and the *DOUT* register is used by the processor to provide data that can be stored outside the processor. One use of the *ADDR* register is for reading, or *fetching*, instructions from memory; when the processor wants to fetch an instruction, the contents of *PC* (*R7*) are transferred across the bus and loaded into *ADDR*. This address is provided to memory. In addition to fetching instructions, the processor can read data at any address by using the *ADDR* register. Both data and instructions are read into the processor on the *DIN* input port. The processor can write data for storage at an external address by placing this address into the *ADDR* register, placing the data to be stored into its *DOUT* register, and asserting the output of the *W* (write) flip-flop to 1.

Figure 12 illustrates how the enhanced processor is connected to memory and other devices. The memory unit in the figure supports both read and write operations and therefore has both address and data inputs, as well as a write enable input. The memory also has a clock input, because the address, data, and write enable inputs must be loaded into the memory on an active clock edge. This type of memory unit is usually called a *synchronous static random access memory* (*synchronous SRAM*). Figure 12 also includes a 9-bit register that can be used to store data

from the processor; this register might be connected to a set of LEDs to allow display of data on your DE-series board. To allow the processor to select either the memory unit or register when performing a write operation, the circuit includes some logic gates that perform *address decoding*: if the upper address lines are $A_8A_7 = 00$, then the memory module will be written at the address given on the lower address lines. Figure 12 shows n lower address lines connected to the memory; for this exercise a memory with 128 words is probably sufficient, which implies that $n = 7$ and the memory address port is driven by $A_6 \dots A_0$. For addresses in which $A_8A_7 = 01$, the data written by the processor is loaded into the register whose outputs are called *LEDs* in Figure 12.

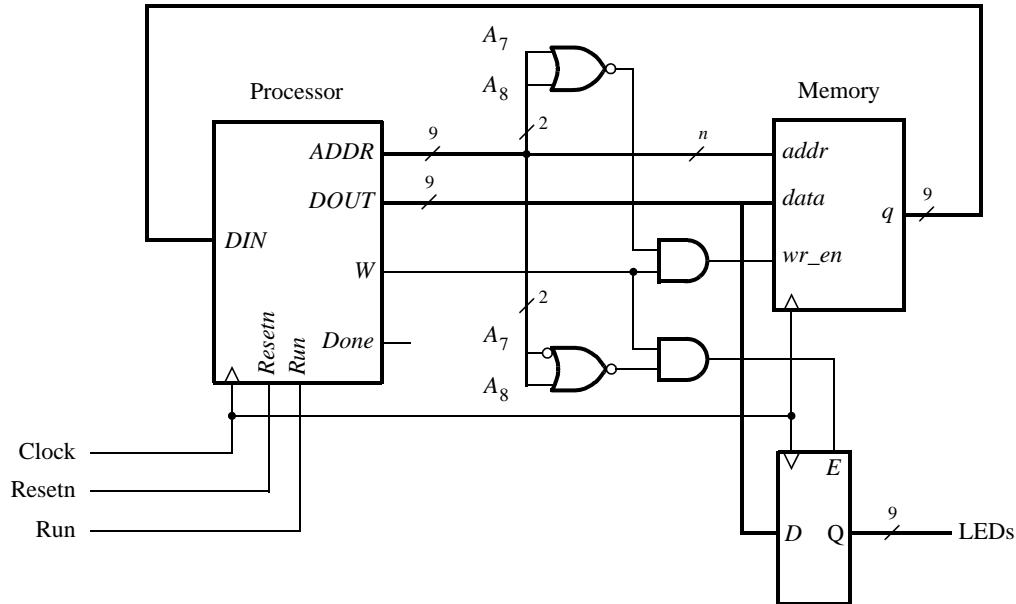


Figure 12: Connecting the enhanced processor to a memory and output register.

1. Create a new Quartus project for the enhanced version of the processor.
2. Write Verilog code for the processor and test your circuit by using functional simulation: apply instructions to the *DIN* port and observe the internal processor signals as the instructions are executed. Pay careful attention to the timing of signals between your processor and external memory; account for the fact that the memory has registered input ports, as we discussed for Figure 12.
3. Create another Quartus project that instantiates the processor, memory module, and register shown in Figure 12. Use the Quartus IP Catalog to create the RAM: 1-PORT memory module. Follow the instructions provided by the wizard to create a memory that has one 9-bit wide read/write data port and is 128 words deep. Ensure that the output is not registered. Use a MIF file to store instructions in the memory that are to be executed by your processor. An example program in the form of a MIF file is shown in Figure 13. This program display an 8-bit counter value on the LEDs output port. Loops are used in the program to create delays so that the counter values are not changed too quickly to be observed. Comments are included in the MIF file in Figure 13 to describe the program's code.
4. Use functional simulation to test the circuit. Ensure that data is read properly from the memory and executed by the processor.
5. Include in your project the necessary pin assignments to implement your circuit on your DE-series board. Use switch SW_9 to drive the processor's *Run* input, use KEY_0 for *Resetn*, and use the board's 50 MHz clock signal as the *Clock* input. Since the circuit needs to run properly at 50 MHz, make sure that a timing constraint is set in Quartus to constrain the circuit's clock to this frequency. Read the Report produced by the Quartus Timing Analyzer to ensure that your circuit operates at this speed; if not, use the Quartus tools to analyze your circuit and modify your Verilog code to make a more efficient design that meets the

50-MHz speed requirement. Also note that the *Run* input is asynchronous to the clock signal, so make sure to synchronize this input using flip-flops.

Connect the *LEDs* register in Figure 12 to *LEDR₈₋₀* so that you can observe the output produced by the processor.

6. Compile the circuit, download it into the FPGA chip, and ensure that your program runs properly.

```

DEPTH = 128;
WIDTH = 9;
ADDRESS_RADIX = HEX;
DATA_RADIX = BIN;
CONTENT
BEGIN

% This code displays a count (in register R2) on the red LEDs.                                %
00 : 001001000; %          mvi    R1,#1          // initialize R                                %
01 : 000000001;
02 : 001010000; %          mvi    R2,#0          // counter to display on LEDs                %
03 : 000000000;
04 : 001011000; % Loop    mvi    R3,#010000000    // R3 = address of LEDs register          %
05 : 010000000;
06 : 101010011; %          st     R2,R3          // write to LEDs                            %
07 : 010010001; %          add    R2,R1          // increment counter for LEDs                %
08 : 001011000; %          mvi    R3,#111111111    // delay value                            %
09 : 111111111;
0A : 000101111; %          mv     R5,R7          // save address of next inst.                %
0B : 001100000; % Outer   mvi    R4,#111111111    // nested delay loop                    %
0C : 111111111;
0D : 000000111; %          mv     R0,R7          // save address of next inst.                %
0E : 011100001; % Inner   sub     R4,R1          // decrement loop delay variable            %
0F : 110111000; %          mvnz   R7,R0          // continue Inner loop if R4 !=0            %
10 : 011011001; %          sub     R3,R1          // decrement outer loop delay              %
11 : 110111101; %          mvnz   R7,R5          // continue Outer loop if R3 !=0            %
12 : 001111000; %          mvi    R7,#Loop        // execute again                          %
13 : 000000100;

END;
```

Figure 13: An example program in a memory initialization file (MIF).

Part IV

In this part you are to connect an additional I/O module to your circuit from Part III and write code that is executed by your processor.

Add a module called *seg7_scroll* to your circuit. This module should contain one register for each 7-segment display on your DE-series board. Each register should directly drive the segment lights for one 7-segment display, so that the processor can write characters onto these displays. Create the necessary address decoding to allow the processor to write to the registers in the *seg7_scroll* module.

1. Create a Quartus project for your circuit and write the Verilog code that includes the circuit from Figure 12 in addition to your *seg7_scroll* module.

2. Use functional simulation to test the circuit.
3. Add appropriate timing constraints and pin assignments to your project, and write a MIF file that allows the processor to write characters to the 7-segment displays. A simple program would write a word to the displays and then terminate, but a more interesting program could scroll a message across the displays, or scroll a word across the displays in the left, right, or both directions.
4. Test the functionality of your design by executing code from the memory and observing the 7-segment displays.

Part V

Add to your circuit from Part IV another module, called *port_n*, that allows the processor to read the state of some switches on the board. The switch values should be stored into a register, and the processor should be able to read this register by using a **ld** instruction. You will have to use address decoding and multiplexers to allow the processor to read from either the memory or *port_n* units, according to the address used.

1. Draw a circuit diagram that shows how the *port_n* unit is incorporated into the system.
2. Create a Quartus project for your circuit, write the Verilog code, and write a MIF file that demonstrates use of the *port_n* module. One interesting application is to have the processor scroll a message across the 7-segment displays and use the values read from the *port_n* module to change the speed at which the message is scrolled.
3. Test your circuit both by using functional simulation and by downloading it and executing your processor code on your DE-series board.

Suggested Bonus Parts

The following are suggested bonus parts for this exercise.

1. Use the Quartus tools to identify the critical paths in the processor circuit. Modify the processor design so that the circuit will operate at the highest clock frequency that you can achieve.
2. Extend the instructions supported by your processor to make it more flexible. Some suggested instruction types are logic instructions (AND, OR, etc), shift instructions, and branch instructions. You may also wish to add support for logical conditions other than “not zero”, as supported by **mvnz**, and the like.
3. Write an Assembler program for your processor. It should automatically produce a MIF file from assembly language code.

Copyright © 1991-2016 Intel Corporation. All rights reserved. Intel, The Programmable Solutions Company, the stylized Intel logo, specific device designations, and all other words and logos that are identified as trademarks and/or service marks are, unless noted otherwise, the trademarks and service marks of Intel Corporation in the U.S. and other countries. All other product or service names are the property of their respective holders. Intel products are protected under numerous U.S. and foreign patents and pending applications, mask work rights, and copyrights. Intel warrants performance of its semiconductor products to current specifications in accordance with Intel's standard warranty, but reserves the right to make changes to any products and services at any time without notice. Intel assumes no responsibility or liability arising out of the application or use of any information, product, or service described herein except as expressly agreed to in writing by Intel Corporation. Intel customers are advised to obtain the latest version of device specifications before relying on any published information and before placing orders for products or services.

This document is being provided on an "as-is" basis and as an accommodation and therefore all warranties, representations or guarantees of any kind (whether express, implied or statutory) including, without limitation, warranties of merchantability, non-infringement, or fitness for a particular purpose, are specifically disclaimed.